

EEC0055 - Digital Systems Design

2018/2019

Laboratory 3

19 November - ~~21 December 2018~~ (new due date: 11 January 2019)

All-digital FM stereo modulator

Version 0.4 - 13 December 2018

Revision history

| date | notes | author |
|----------------------|---|--|
| V0.1 Nov 18, 2018 | First version | jca@fe.up.pt |
| V0.2 Nov 23, 2018 | Added section 3.2.1 Verification kit for the generic DDS module; Modified section 3.1, changing the specification of the main clock frequency to 147.456000 MHz (integer multiple of 48 kHz); | jca@fe.up.pt |
| V0.3 Nov 26, 2018 | Added section 4 - IP cores, with the description of the two intellectual property blocks provided for the FM modulator implementation: sequential multiplier and 4X interpolator | jca@fe.up.pt |
| V0.4 Dec 13, 2018 | Added section 5 with the description of the verification environment provided (Verilog testbench and Matlab/Octave programs) Added section 6 with updates to the initial specification and additional implementation details The due date has been updated to January 11 th , 2019 | jca@fe.up.pt |

1 - Introduction

In this project the students will implement a FM stereo modulator and transmitter. The input stereo audio signal is received from an audio source connected to the Line-in or Mic-in inputs of the Atlys board. These analog signals are digitized by an audio codec on the board. Inside the reference project provided for the Atlys board, where your design will be implemented, the digital audio signal is already available as two 18-bit signed words sampled at 48 kHz. The same serial interface implemented in the previous projects will be used in this design to configure some parameters of the FM modulator.

Your design will receive the stereo high-quality digital audio signal, generate the multiplexed FM-stereo signal to modulate in frequency a 5 MHz sinusoidal signal, sampled at 160 MHz. The digital output (8 bits) will be connected to an external digital to analog converter (DAC) that will produce an FM analog signal sampled at 100 Mhz. A FM radio receiver placed nearby the transmitter and tuned to 95 MHz or 105 MHz will be able to receive the FM signal.

Figure 1 shows the overall organization of the system. The FM modulator (block FMSTEREO) is detailed in the next section and a complete Matlab will be provided for generating golden simulation data for each of the blocks.

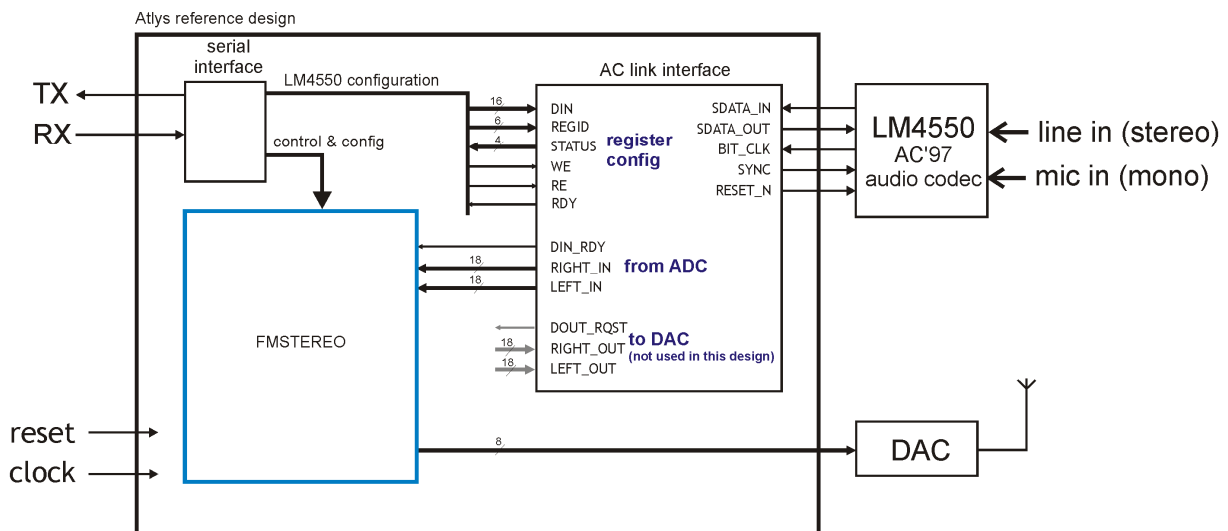


Figure 1 - Simplified block diagram of the reference project. The design to develop is represented by the block FMSTEREO.

2 - FM and FM stereo basics

This section introduces the basics concepts of frequency modulation and the process of encoding the two channels of a stereo signal. If you are familiar with these concepts you can skip this section.

2.1 - Frequency modulation

FM or frequency modulation is a process to encode analog information (a low frequency audio signal (t)) on a high frequency carrier signal (for example the FM broadcast radio signal in the band 88 - 108 MHz). In a FM signal, the instantaneous frequency is a fixed value ω_c (the frequency tuned to listen to a FM radio station) summed to a deviation in frequency that is proportional to the amplitude of the encoded signal $m(t)$. The FM modulation used in the commercial FM broadcast in Europe uses a maximum frequency deviation of ± 50 kHz.

The instantaneous angular frequency of a FM signal $\omega_i(t)$ is thus defined as:

$$\omega_i(t) = \omega_c + K_f m(t) \quad (1)$$

where K_f is a frequency deviation constant that depends on the maximum amplitude of the signal $m(t)$.

A sinusoidal signal with constant angular frequency ω_c is represented by:

$$x(t) = A \cdot \cos(\omega_c t) = A \cdot \cos(\theta(t)) \quad (2)$$

where $\omega_c t = \theta(t)$ is the instantaneous angle argument of the cosine function. If the frequency varies with time, as $\omega_i(t)$ in equation 1, the angle argument of the cosine function is the integral with time of that frequency:

$$\theta(t) = \int_{-\infty}^t \omega_i(\alpha) d\alpha = \int_{-\infty}^t (\omega_c + K_f m(\alpha)) d\alpha \quad (3)$$

The process to generate a FM signal uses directly the relationship in equations 2 and 3: the output signal is the cosine of an angle $\theta(t)$ obtained by accumulating along time a constant ω_c added to the signal to modulate.

2.2 - FM Stereo

A FM stereo broadcast encodes a two channel audio signal by calculating the sum of the two channels $L + R = (left(t) + right(t))$ and the difference between them $L - R = (left(t) - right(t))$. The signal $m(t)$ is obtained by summing $L + R$, $L - R$ multiplied by a 38 kHz sine wave and a 19 kHz pilot sine wave (the constants K_s , K_d and K_p will be defined later).

$$m_{stereo}(t) = K_s(left(t) + right(t)) + K_d(left(t) - right(t)) \times \cos(2\pi \times 38k t) + K_p \cos(2\pi \times 19k t)$$

Figure 2 shows the spectrum of a FM stereo signal.


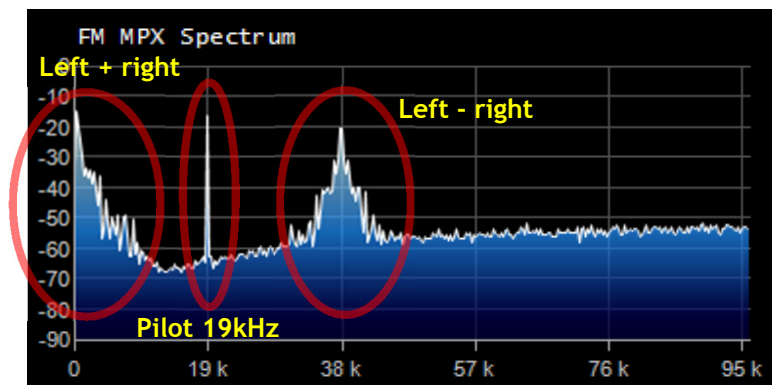


Figure 2 - Spectrum of a FM stereo signal (image created by the software-radio application SDRSharp - free download from airspy.com)

3 - Digital implementation

The construction of the FM stereo modulator requires the implementation of 3 different cosine functions, two with constant frequencies (19 kHz and 38 kHz) and one with the angular argument defined by equation 3. This is thus a fundamental building block for our system and we will start by implementing a parameterizable digital system to generate a sinusoidal wave.

One process to implement a digital calculator of the function $\cos(x)$ is called Direct Digital Synthesizer (DDS¹, see figure 3) and is based on a look-up table (a ROM-like memory) holding N equally spaced samples of one period of the function cosine (or any other periodic function). That memory is addressed by an accumulator register whose instantaneous value represents the angle argument of the cosine. The step of increment of the accumulator (the value accumulated at each clock cycle) dictates the frequency of the output cosine function. To generate the FM signal, that step must be proportional to $\omega_c + K_f m(t)$.

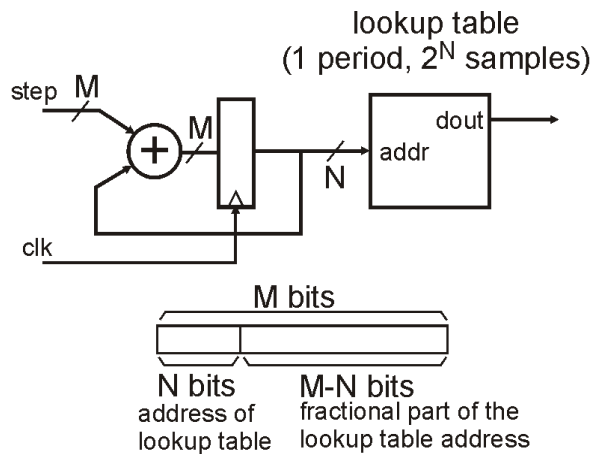

The frequency of the output wave is determined by equation 4, where F_{sine} represents the frequency of the output signal and F_{clk} is the clock frequency.

$$F_{\text{sine}} = \frac{F_{\text{clk}}}{2^N} \times \text{step} \quad (4)$$

Input **step** is a fixed point value with N integer bits and (M-N) fractional bits, defining the phase increment for each clock cycle.

Figure 3 - Direct Digital Synthesizer

Figure 4 presents a simplified block diagram of the complete FM stereo modulator. The target clock frequency will be 160 MHz and the whole circuit should be synchronous with the main clock, using a global synchronous reset.

The input signals (the left and right audio channels) are available as 18 bit two's complement words sampled at 48 kHz. Signals **LpR** and **LmR** (addition and subtraction of the two input channels) are multiplied by the constants **Ks** and **Kd** (4 bit unsigned) representing positive numbers between 0 (0.000b) and 1.875 (1.111b). The results of these multiplications are scaled to 18 bits and up-sampled to $4 \times 48\text{kHz} = 192\text{ kHz}$ using a first-order interpolator (this block will be available as a RTL Verilog module). The **LmR** signal is then multiplied by a 38 kHz cosine function generated by a DDS, using the same 192 kHz sampling frequency. The result of this multiplication is scaled down again to fit into 18 bits. Finally, the **mstereo** signal is constructed by adding the scaled **LpR** signal, the **LmR** multiplied by the 38 kHz cosine and the output of a second DDS generating a 19 kHz cosine function. The output of this addition is scaled down to fit the 20 bit dynamic range.

The FM modulation is performed by a third DDS, where the accumulator increment **Phase** is a linear function of the **mstereo** signal: **Phase** = **stepWc** + **mstereo** * **Kf**. This DDS will have a lookup-table with 32 entries (for the whole cosine period), holding samples with 8 bits in two's complement signed format. With **stepWc**=1 and the clock frequency equal to 160 MHz, the central frequency of the output sine wave will be 5 MHz. The output of this DDS is applied to an external digital to analog converter to generate the output analog signal.

The parameters **Ks**, **Kd**, **Kp**, **Kf** and **stepWc** will be provided by output ports of the serial interface. Additional ports can be used to configure other parameters of your design.

¹ A brief introduction to DDS can be found in http://ftp.ni.com/evaluation/pxi/Direct_Digital_Synthesis.pdf

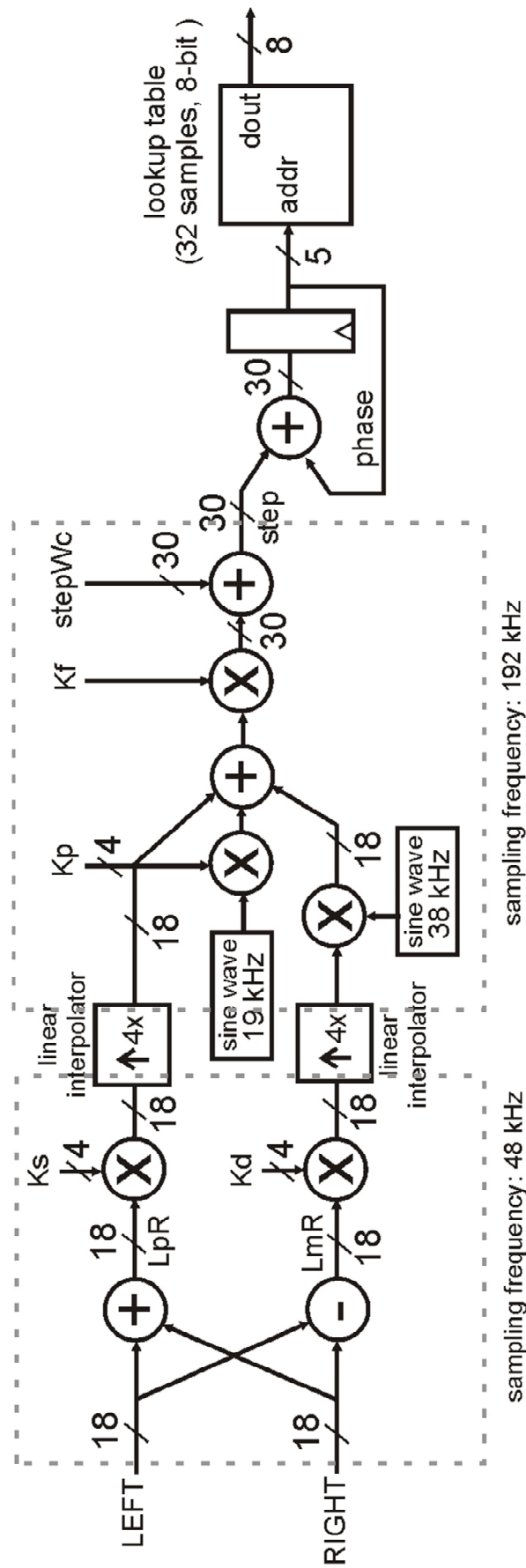


Figure 4 - FM stereo digital modulator

3.1 Design goals and constraints

The global design goal should be to minimize the area, measured as the number of lookup tables and flip-flops. The arithmetic blocks available in the FPGA (DSP48) should not be used in this design. A small sequential multiplier will be available to implement the multiplications shown in the datapath.

The clock frequency of the final DDS should be 147.456000 MHz. The rest of the circuit can use that same clock frequency (the easiest solution) or slower clocks with frequencies adjusted to the requirements of each section. This later option is more challenging as it requires to solve the clock domain crossing (CDC) synchronization issues. Note that a 48 kHz clock would be sufficient for the initial section before the interpolators, but in that case combinational (and large) multipliers need to be used.

3.2 Development stages - generic DDS

The first block to develop is a parameterizable digital sine wave generator, using the DDS architecture referred above. Build a Verilog module implementing the circuit represented in figure 2. The same Verilog module should be flexible enough to implement the 3 DDS blocks needed in the FM modulator. The contents of the lookup table can be loaded at compile time from a text file (either for simulation and synthesis) using the Verilog system task `$readmemb ()`. This module must have a clock enable input and a synchronous reset.

3.2.1 Verification kit for the generic DDS module

This verification kit is prepared to perform the logic simulation the Verilog module that implements the DDS sine generator. This is provided as a set of files organized with the same directory structure used for the previous projects. The kit contains:

| | |
|--|--|
| <code>./matlab/dds.m</code> | Matlab/Octave script to create the simulation data required for the testbench and to analyse the sine wave for different configurations of the DDS parameters; |
| <code>./simdata</code> | The script <code>dds.m</code> will create in this directory two data files that will be used by the Verilog testbench; |
| <code>./src/verilog-tb/dds_tb.v</code> | The testbench to perform the functional and the post-synthesis simulation; |

To use this kit **you must follow exactly the instructions below** (this same text is included in the beginning of the testbench `dds_tb.v`):

1. Edit the script `./matlab/dds.m` and adjust the following parameters to match the DDS configuration you want to verify:

```
duration = 0.1;    % Duration of the output test signal (seconds):
Fs = 192000;       % Sampling frequency (Hz):
Fout = 19000;      % required output frequency (Hz):
Nbits_sine_LUT = 9; % Number of bits per sample in lookup-table
Nsamples_LUT = 128; % Number of samples in the lookup-table (int power of 2)
Nfrac = 6;         % Number of bits of the fractional phase:
                  % note that the number of bits in the integer part of the
                  % phase is given by log2( NsamplesLUT )
```

2. Run the script `dds.m` in Matlab/Octave, in directory `./matlab`. This will generate the data for the DDS lookup table (file `./simdata/DDS_LUT.hex`) and a vector with the output sine samples generated by the DDS (file `./simdata/DDSout.hex`). These files are ASCII with one signed data sample per line in hexadecimal format and the high-order bits to

the left of the Nbits_sine_LUT bit padded with zeros (only the lower Nbits_sine_LUT are meaningful). To use the DDSLUT.hex file to load your lookup-table (register array sineLUT), you can include the following Verilog code into your module:

```
reg [31:0] sineLUT[ 0 : Nsamples_LUT-1 ];  
initial  
    $readmemh("../simdata/DDSLUT.hex", sineLUT );
```

The lookup-table should be defined as a 32-bit register array, even if the data samples use less bits. The output port of the DDS module should only output the meaningful bits. This script also outputs the required phase increment for the output frequency set.

Register this number as it will be necessary to configure the parameter PHASE_INCREMENT in the testbench

3. Adjust the following simulation parameters in the testbench:

```
parameter FS          = 192000; // Sampling frequency  
parameter MAX_SIM_SAMPLES = 19200; // Maximum simulation time is 0.1 second  
parameter N_OUTPUT_BITS = 9;      // Number of valid bits in the output word  
parameter PHASE_INCREMENT = 32'b001100_101010; // 12.6562500 in binary: 001100.101010  
                                              // for generate a 19 kHz sine wave
```

4. Set up and run the simulation in QuestaSim:

4.1 Create a QuestaSim project in ./sim

4.2 Import to the project your dds.v and this testbench (./src/verilog-tb/dds_tb.v). You may need to adjust the module and signal names and define the parameters needed to configure your module: number of samples in the DDS LUT, number of bits per sample and number of bits of the fractional part of the phase. Note that the example of instantiation included in this testbench does not define any parameter.

4.3 The testbench compares automatically the results generated by the DDS module with the results generated by the Matlab script. If errors are found and you need to analyse the signals in more detail, the signal 'outsineNbits' contains the output with only the number of bits defined by parameter 'Nbits_sine_LUT'. This signal can be plotted in the waveform window using radix decimal and format analog.

4.4 If no errors are reported for the various configurations needed, congratulations! You have created a fundamental building block of the FM modulator.

5. If the simulation succeed, you can proceed with the RTL synthesis and post-synthesis verification, using this same testbench (refer to the guide of laboratory project 2).

4 - IP blocks

Two IP (*intellectual property*) blocks are made available for free: a signed multiplier and a 4X linear interpolator. These are provided as Verilog RTL synthesizable modules, including very basic testbenches to illustrate the module instantiation and the respective eco systems. These modules are available in directory ./IP-cores/seqmultNM and ./IP-cores/interpol4x.

4.1 - Sequential signed multiplier - module seqmultNM (seqmultNM.v)

The sequential signed multiplier implements the shift-add sequential multiplication algorithm in $N+2$ clock cycles (N is the number of bits of the multiplier). The module is instantiated as:

```

seqmultNM    #(          // definition of parameters
                .N( N ), // parameter N = number of bits of the multiplier
                .M( M )  // parameter M = numero of bits of the multiplicand
            )
seqmult_1    // instance name
(
    .clock( clock ), // Master clock
    .reset( reset ), // Master reset, synchronous and active high
    .start( start ), // Set to 1 during one clock cycle to start the multiplication
    .ready( ready ), // Set to 1 when the multiplier is ready to accept a new start
    .A( A ),         // Multiplicand, signed   M bits
    .B( B ),         // Multiplier, signed   N bits
    .R( R )          // Result, signed      M+N bits
);

```

The module receives two parameters to specify the number of bits of the multiplicand (parameter **M**) and the number of bits of the multiplier (parameter **N**). This module requires **N+2** clock cycles to complete one multiplication and the signed result has **N+M** bits. Setting input **start** to 1 during one clock cycle will load the operands **A** and **B** (multiplicand and multiplier, respectively) and start the shift-add iterative process. When the iterative process is running, the output **ready** is set to 0 and returns to 1 when the multiplication ends. The result is ready at output **R** when output **ready** is 1 after an activation of **start**. While the process is running, the output **R** has meaningless data.

Figure 5 shows the simulation waveforms for a multiplication with a 14 bit multiplicand (input **A**) and a 12 bit multiplier (input **B**). The result in output **R** is ready **N+2** clock cycles after **start** is set.

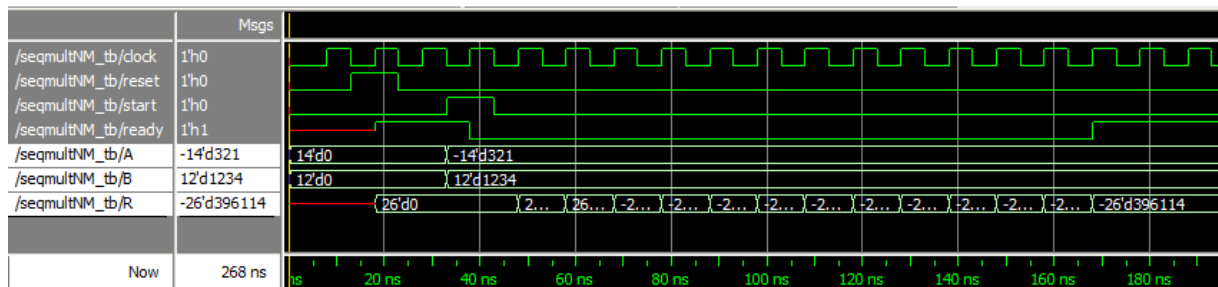


Figure 5 - Example of simulation waveforms for the sequential multiplier.

4.2 - Linear interpolator x4 - module interpol4x (interpol4x.v)

The linear interpolator receives a stream of 18-bit samples (input **xkin**) sampled at a rate defined by the clock enable signal **clkenin** and generates a stream of 18-bit samples (output **ykout**) with a sampling frequency determined by the clock enable signal **clken4x**. The output sampling frequency must be exactly 4 times higher than the input sampling frequency and the additional samples at the output are obtained by the linear interpolation between each two samples of the input stream.

The module can be instantiated as:

```
interpol4x
interpol4x_1(
    .clock( clock ),          // Master clock
    .reset( reset ),          // Master reset, synchronous active high
    .clkenin( en48000Hz ),    // Input clock enable
    .clken4x( en192000Hz ),    // Output clock enable (4X the input enable)
    .xkin( xkin ),             // Input signal, 18 bit signed
    .ykout( ykout )            // Output signal, 18 bit signed
);
```

Signals **clkenin** and **clken4x** are clock enable signals (active only during one clock cycle) whose frequencies dictate the input sampling rate and the output sampling rate. In your design these frequencies will be 48 kHz and 192 kHz.

Figure 6 shows in detail the relationship between the two clock enable signals and figure 7 presents a simulation waveform created with the simple testbench included in the kit. To observe the analog view, configure the signal with radix decimal (signed, two's complement) and format analog (set the maximum and minimum values in the signal and the height of the display window reserved for that signal).

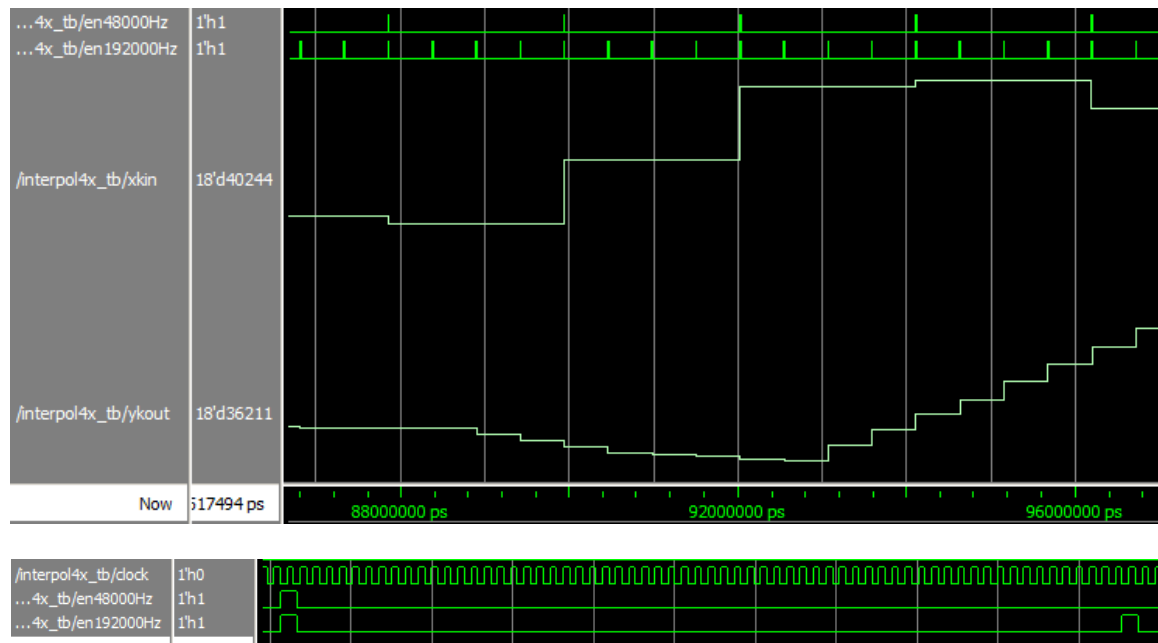


Figure 6 - Example of simulation waveforms for the 4X interpolator - relationship between the two clock enable signals.

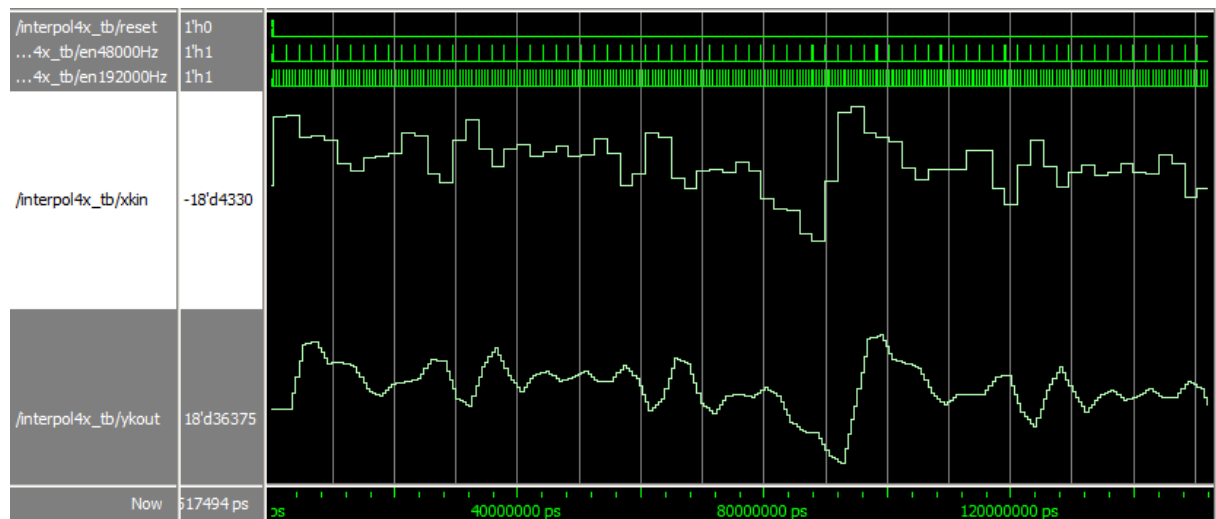


Figure 7 - Example of simulation waveforms for the 4X interpolator - input signal samples at F_s and output signal sampled at $4x F_s$ with linear interpolation.

5 - Verification environment

The verification of the RTL model is done with a self-checking testbench (Verilog) and a set of Matlab/Octave scripts to generate and process various data files required for setting up and running the logic simulation of the RTL model.

This verification environment applies to the signal at the output of the multiplier by the gain K_f (see figure 9 below, signal **FMout**). If you have already implemented the whole system, you should add one additional output to bring out the signal at this point. If you did not yet finish the model, ignore for now the final DDS and the adder with **stepWc**.

The diagram in figure 8 illustrates the verification flow that is further detailed below.

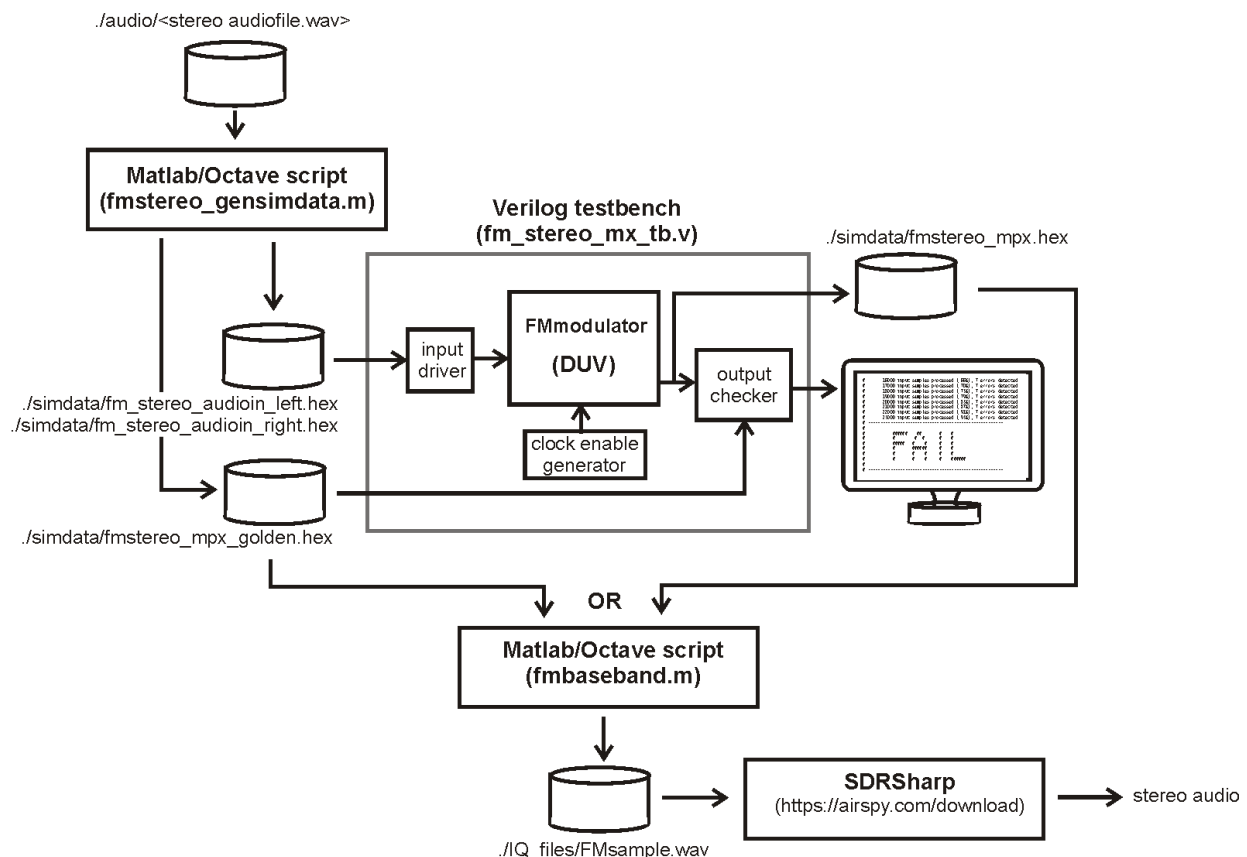


Figure 8 - Verification flow. The Matlab/Octave script fmbaseband.m implements the final FM modulation performed by the final DDS, not considered for this verification process.

- i) Run the Matlab/Octave script `./matlab/fmstereo_gensimdata.m`. To run in Octave you may need to uncomment the statement “`pkg load signal`” (around line 4). Before running the script, you should configure some parameters, between lines 1 and 30, mainly the 4 gains that will be the inputs of your module. Note that these gains must have the bit width referred in the program and must be set accordingly (lines 13 - 16). The data filenames may also be changed (not needed and not recommendable). This program executes the following main tasks:
 1. reads a stereo audio file (some audio samples available in `./audio`);
 2. resamples the audio data to 48 kHz;
 3. generates two text files in hexadecimal format with the audio samples quantized to 18 bits, to be read by the Verilog testbench with the tasks `$readmemh()`. The default filenames for these files are `./simdata/fmstereo_audioin_left.hex` and `./simdata/fmstereo_audioin_right.hex`;
 4. executes a functional model of the FM stereo modulator, using the same parameters specified for the digital implementation: bit widths, truncation of fractional parts, configuration of the DDS modules and interpolator. The final result generated by this program should be equal bit-by-bit to the output of the RTL model;
 5. creates a text file with the correct results, in hexadecimal format. The default filename of this file is `./simdata/fmstereo_mpx_golden.hex`.
- ii) Edit the toplevel testbench `./src/verilog-tb/fm_stereo_mx_tb.v`, read the comments in the section defining the parameters (lines 1 - 64), configure the simulation parameters and the gains (note the filenames and gains must be the same as in the Matlab/Octave script), and run a simulation with QuestaSim or any other Verilog simulator.

You can run QuestaSim without using the GUI by executing the command “**make**” in directory `./sim` (you need the Cygwin environment that should be already installed in the PCs of the lab). Look at `./sim/Makefile` to understand how to launch a simulation from the command line. File `./sim/vlogfiles` contain the list of Verilog filenames to compile for running the simulation in batch mode. The current file only compiles the source Verilog files provided and uses the pre-compiled modules of the reference FM modulator and the DDS blocks. With these modules you can experiment simulating the testbench and playing with some of the configuration parameters. To simulate with your modules, edit `./sim/vlogfiles` and correct the filenames to match your design hierarchy.

To run QuestaSim with the GUI you can open the simulation project in `./sim/fmmulator.mpf`. This project only compiles the provided source files and uses the pre-compiled models of the reference FM modulator and DDS blocks.

The testbench reads the two data files generated by the Matlab/Octave program, with the input data samples of the left and right audio signal, applies the samples to the corresponding inputs of the RTL module synchronized with the 48 kHz clock enable signal, captures the output and compares it with the corresponding expected sample read from the golden file created by the Matlab/Octave model.

- iii) Run the simulation. The testbench implements a self-checking process and if no error is found nothing more is reported than a final “Pass”. If errors are found, the first errors are reported and the simulation is stopped after a certain number of errors is found. Here begins the hard task of debugging your digital design!

6 - Updates to the initial specification and additional implementation details

This section updates some specifications and provides additional information about the design implementation. Figure 10 highlights the bus widths of the 192 kHz section.

Clock frequency: the main clock frequency will be equal $48000 \times 2048 = 98\,304\,000$ MHz (period 10.173 ns), which is convenient for generating the final FM signal.

DDS modules: the two DDS modules for the 19 kHz and 38 kHz sine waves should be configured with the following parameters (refer to section 3.2.1).

- LUT size (one full period): 64 samples
- Sample width: 8 bits, signed, two's complement
- Fractional part of the phase: 12 bits

Gain Kf: the gain Kf must be 8 bits (unsigned), with 4 bits for the fractional part.

Gain Kp: this gain is 4 bits (the 3 least significant bits represent fractional bits). The 8-bit output of the 19 kHz sine generator must be multiplied by the 4-bit integer Kp and then scaled up to the 18-bit dynamic range by multiplying again by 2^6 (adding 6 zeros at the right).

Multiplication by the 38 kHz sine: the multiplication of the 8-bit output of the 38 kHz sine wave generator by the 18-bit output of the linear interpolator of the left-right path should be scaled down to 18 bits by dividing the result of the multiplication by 2^8 .

Final summation: the addition of the three components produces a result that will fit into 20 bits. No scaling is necessary at this point.

Multiplication by gain Kf: the gain Kf is 8 bit wide (unsigned) with 4 bits representing the integer part and 4 bits the fractional part. The result of the multiplication must then discard

(truncate) the 4 least significant bits to fit the final result in 24 bits. This is the final result that will be verified by the verification environment described in the section 5.

Clock enable generator: a new module (`./IP-cores/clockenablegen.v`) is included that implements a generator of the two clock enables required by the design. This is configurable with two parameters that define the relative timing of the 48 kHz and 192 kHz clock enable pulses (do not modify these parameters unless you know exactly what you are doing and you really need to do that). This module is instantiated in the testbench (between lines 140 and 150) and the Verilog file contains a brief description of the timing between these two signals.

Signed/unsigned multiplications: the sequential multiplier provided implements signed, two's complement multiplications. When multiplying signed data by a word representing unsigned data (as the K gains in this design), this word must be extended by concatenating a zero at the left to represent the same unsigned value but as a positive number. For example, if an unsigned 4-bit word is equal to 1110b its value is 14 decimal but if it is used as a 4-bit operand of a signed multiplier it will be processed as -2 decimal. Adding an extra zero at the left gives 01110b representing +14 decimal as a signed two's complement number.

Truncation of fractional parts: the fractional parts that result from the multiplications by fractional gains (Ks, Kd, Kp and Kf) should always be truncated by discarding the least significant bits. No rounding should be implemented at any point, otherwise the output will not match the result of the Matlab/Octave model and the verification will fail.

Linear interpolator: The module `./IP-cores/Interpolator-4X/verilog/interp4x.v` contains both the previous model and the new implementation (smaller and does not delay the output as with the previous design). The implementation to use by the Verilog compiler is selected by the definition of the symbols `INTERPOL_MODEL_1` to select the previous implementation or `INTERPOL_MODEL_2` to select the new implementation (this is the default). The current reference model in Matlab only considers the new implementation because the previous design introduced a delay of 6 cycles of the 192 kHz clock enable and this will fail the current verification testbench. If you already used the previous interpolator, it is necessary to compensate this by adding an equal delay at the outputs of the two sine generators. The recommended solution is to use the new model.

Data synchronization and timing along the datapath: The final summation of the three signal components requires that the three operand are correctly synchronized with the sampling clock enable signals, otherwise the verification will fail. To ensure that, the sequence of operations along the datapath should follow the following timing (see figure 9):

- i) The input audio samples are applied to the inputs at the rising edge of the main clock when the 48 kHz clock enable is high; These samples must be processed by the L+R and L-R adders and the gain multipliers in less than 2048 clock cycles, as the interpolator will register its inputs at the next 48 kHz clock enable. This way, there is a budget of 2048 clock cycles to perform these operations (using the sequential multiplier) using as little logic as possible.
- ii) The output of the interpolator and the outputs of the two sine wave generators will be updated at the rising edge of the clock, at every 192 kHz clock enable pulse. The path from these outputs to the final register shown in figure 9 should take no more than 512 clock cycles (the period of the 192 kHz clock enable signal), as the final register is loaded in a 192 kHz clock enable pulse the result of the outputs produced in the previous clock enable pulse. The clock budget to perform these operations (the

datapath section shown in figure 9) is thus 512 clock cycles and you should implement this part also trying to minimize the amount of logic resources.

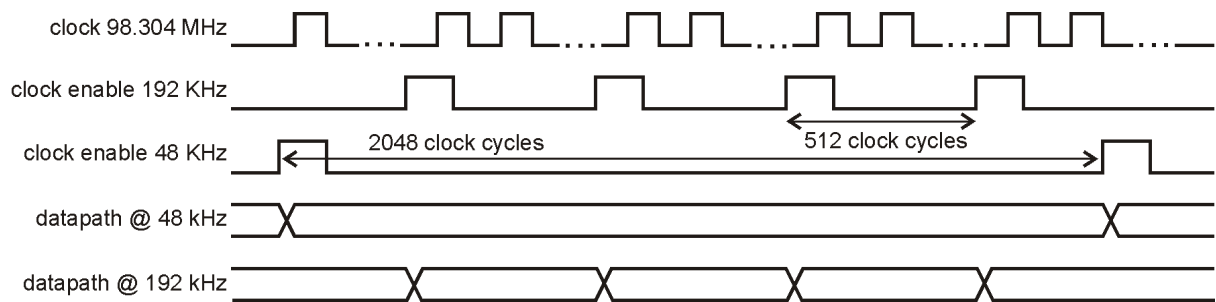


Figure 9 - Timing diagram of the data flow through the datapath.

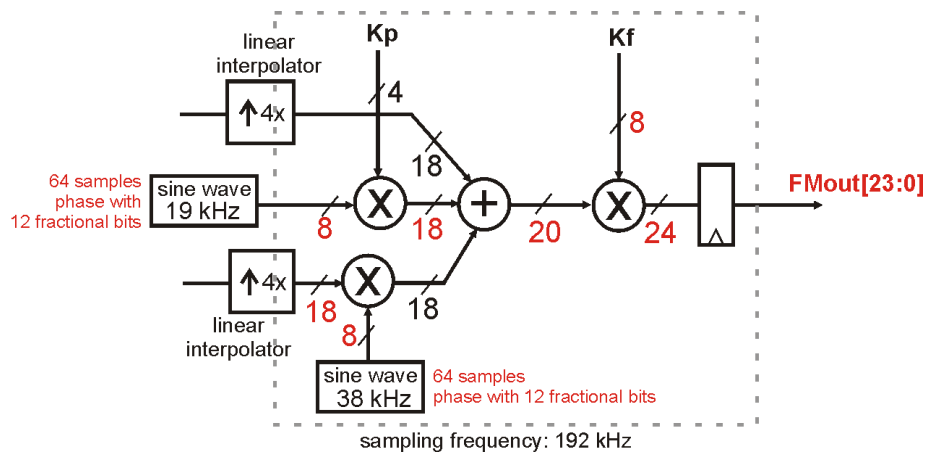


Figure 10 - Updated bus widths of the 192 kHz section. The main output for verification purposes is the signal **FMout**. This signal should be the output of a register enabled by the 192 kHz clock enable.